

Values for Discrete Component Branch Line Coupler (Type-1)

Chris Haji-Michael

<http://www.sunshadow.co.uk/chris.htm>

This page calculates the circuit values for a branch line coupler. The equations are from "Practical Microstrip Circuit Design", Trinogga, Kaizhou, Hunter, P363. In this coupler the wanted power goes from port 1 to port 3; coupled power goes to port 2.

$$\text{Freq} := 2.0 \cdot 10^9 \text{ Hz}$$

$$c := -2, -4, -6, -8, -10, -12, -14, -16 \quad \text{Coupling Ratio (power to port 2 wrt 3)}$$

$$Z_0 := 50 \text{ ohm}$$

$$\text{nH} := 1 \cdot 10^{-9} \text{ H}$$

$$k_2(c) := 10^{\left(\frac{c}{10}\right)} \quad k_3(c) := 1 - k_2(c) \quad k(c) := \frac{k_2(c)}{k_3(c)}$$

$$Z_1(c) := Z_0 \cdot k(c)^{0.5} \quad Z_2(c) := \left[\frac{k(c)}{k(c) + 1} \right]^{0.5} Z_0$$

$$\text{LosstoP3}(c) := 10 \cdot \log(k_3(c))$$


$$L_1(c) := Z_1(c) \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$L_2(c) := Z_2(c) \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_1(c) := \frac{1}{Z_1(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_2(c) := \frac{1}{Z_2(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$C(c) := CL_1(c) + CL_2(c)$$

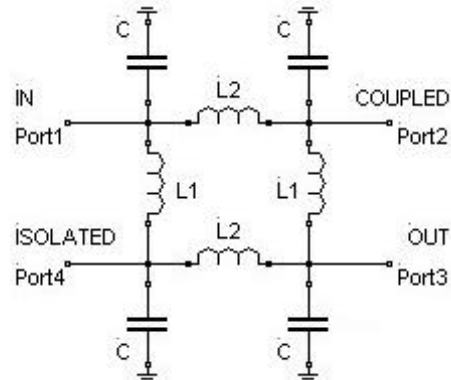

c =	Z1(c) =	Z2(c) =
-2	65.38	39.72
-4	40.66	31.55
-6	28.96	25.06
-8	21.70	19.91
-10	16.67	15.81
-12	12.98	12.56
-14	10.18	9.98
-16	8.03	7.92

Z1 = port 1 to 4 (shunt)
Z2 = port 2 to 3 (series)

Coupling (dB)

Component values

Loss (dB)

c =	L1(c) =	L2(c) =	C(c) =	LosstoP3(c) =
-2	5.20	3.16	3.22	-4.329
-4	3.24	2.51	4.48	-2.205
-6	2.30	1.99	5.92	-1.256
-8	1.73	1.58	7.67	-0.749
-10	1.33	1.26	9.81	-0.458
-12	1.03	1.00	12.47	-0.283
-14	0.81	0.79	15.79	-0.176
-16	0.64	0.63	19.96	-0.110

Simulations for a 10dB coupler

