

# Values for Discrete Component Branch Line Coupler (Type-2)

Chris Haji-Michael

<http://www.sunshadow.co.uk/chris.htm>

This page calculates the circuit values for a branch line coupler. The equations are adapted from "Microwave Engineering using Microstrip", Fooks, Zakarevicius, P158. In this coupler the wanted power goes from port 1 to port 2; coupled to port 3.

$$\text{Freq} := 2.0 \cdot 10^9 \text{ Hz}$$

$$c := -2, -4, \dots, -16 \quad \text{Coupling Ratio (power to port 3 wrt 2)}$$

$$Z_0 := 50 \text{ ohm}$$

$$nH := 1 \cdot 10^{-9} \text{ H}$$

$$k_2(c) := 10^{\left(\frac{c}{10}\right)} \quad k_3(c) := 1 - k_2(c) \quad k(c) := \frac{k_2(c)}{k_3(c)}$$

$$Z_1(c) := \left(\frac{1}{k(c)^{0.5}}\right) \cdot Z_0 \quad Z_2(c) := \left(\frac{1}{k(c) + 1}\right)^{0.5} \cdot Z_0$$

$$\text{LosstoP2}(c) := 10 \cdot \log(k_3(c))$$


$$L_1(c) := Z_1(c) \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$L_2(c) := Z_2(c) \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_1(c) := \frac{1}{Z_1(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$CL_2(c) := \frac{1}{Z_2(c)} \cdot \frac{1}{2 \cdot \pi \cdot \text{Freq}}$$

$$C(c) := CL_1(c) + CL_2(c)$$

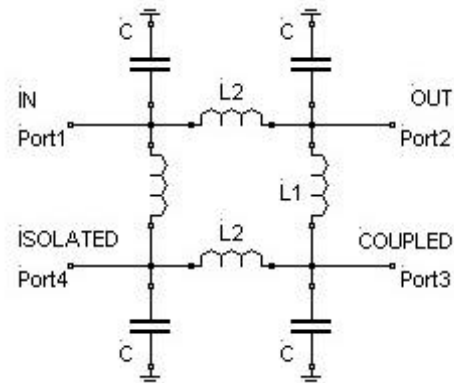

c =	Z1(c) =	Z2(c) =
-2	38.24	30.37
-4	61.48	38.79
-6	86.33	43.27
-8	115.21	45.87
-10	150.00	47.43
-12	192.67	48.4
-14	245.55	48.99
-16	311.49	49.37

Z1 = port 1 to 4 (shunt)  
Z2 = port 2 to 3 (series)



Coupling (dB)

Component values

Loss (dB)

c =	L1(c) =	L2(c) =	C(c) =	LosstoP2(c) =
-2	3.04	2.42	4.70	-4.329
-4	4.89	3.09	3.35	-2.205
-6	6.87	3.44	2.76	-1.256
-8	9.17	3.65	2.43	-0.749
-10	11.94	3.77	2.21	-0.458
-12	15.33	3.85	2.06	-0.283
-14	19.54	3.90	1.95	-0.176
-16	24.79	3.93	1.87	-0.110

### 10dB coupler design

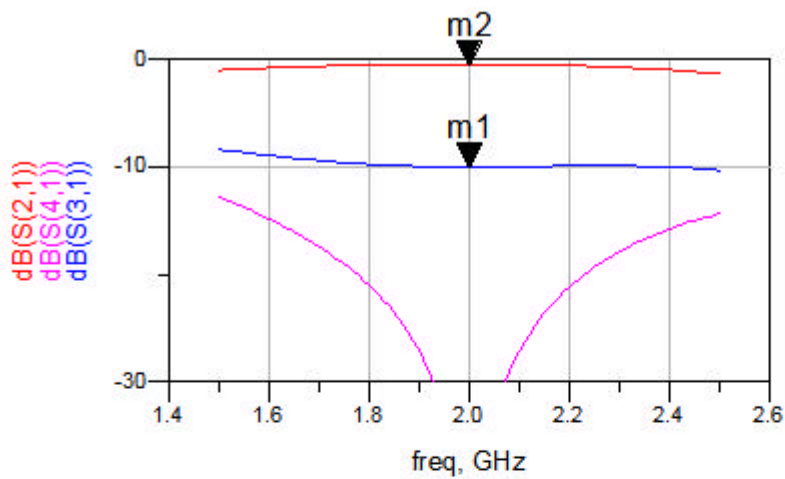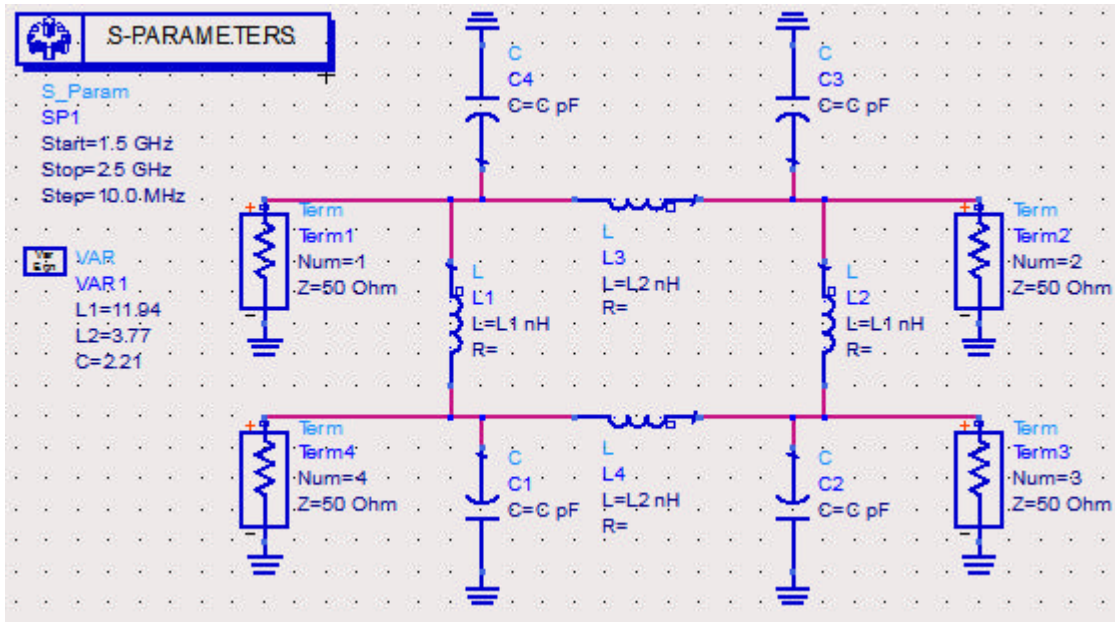

m1  
 freq=2.000GHz  
 dB(S(3,1))=-10.013

m2  
 freq=2.000GHz  
 dB(S(2,1))=-0.456

