
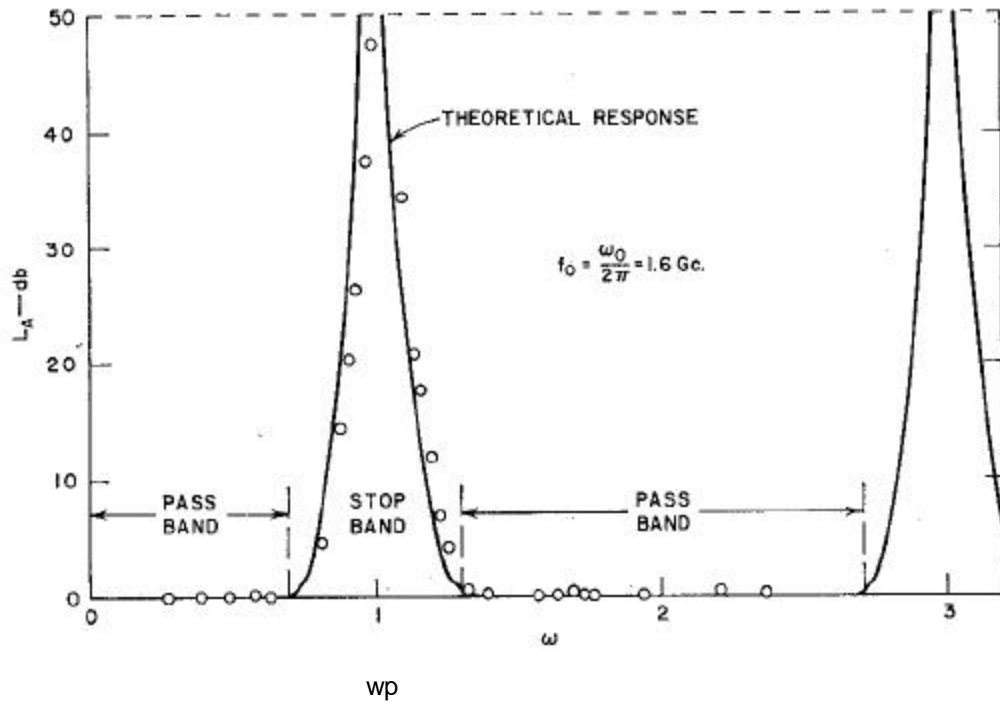


Microwave Notch Filter Design Sheet

Chris Haji-Michael
www.sunshadow.co.uk/chris.htm

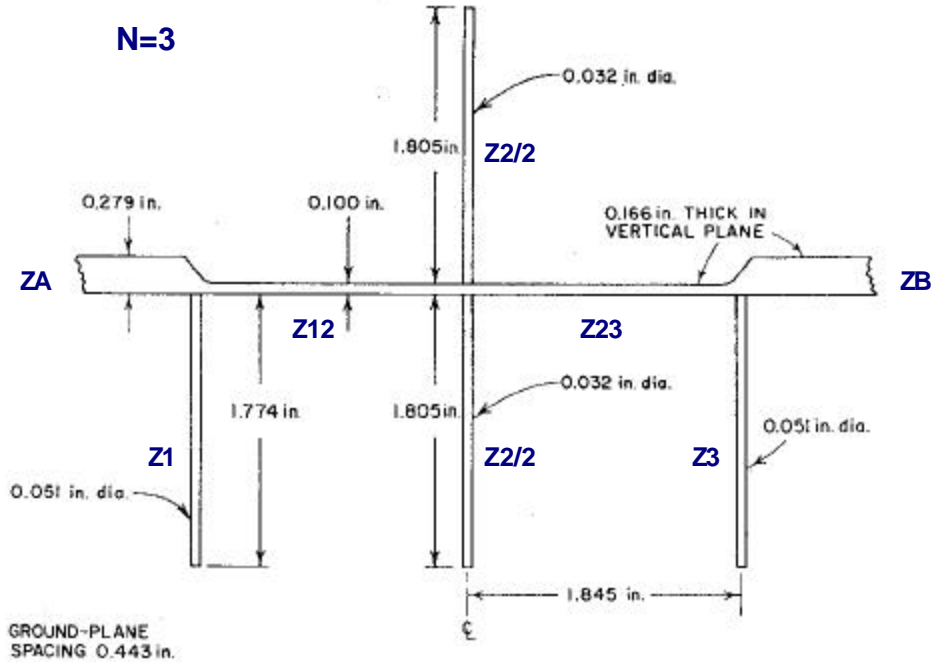This sheet calculates a stop-band filter according to Schiffman and Matthaei, IEEE trans MTT, January 1962. page 6.



There are three steps to this notch filter:

Step 1, Get the filter g-values, this sheet calculated the g values according to the Chebychev polynomial for a given N, but these can be obtained in a variety of ways from books or from a program freely available from this web page.

Step 2, Calculate Zo for the filter (this sheet stops there). All section are lambda/4

Step 3, Calculate length and width. One method is to use Linecalc which is part of ADS. For microstrip designs I have written a MathCAD sheet which is available from my wepage that works well for thin tracks, less well for thicker tracks. Also you can try transcalc.sourceforge.net for a Linecalc equivalent.

Yellow is user input, Green is output

$$\mu\text{m} := 10^{-6} \cdot \text{m} \quad \text{nH} := 10^{-9} \cdot \text{henry}$$

Main user input area:

$L_{\text{ar_db}} := 0.1$ Passband ripple in dB for the chebchev calculations

$N := 5$ Order of the filter 1 to 5, please choose correct section below for the results

$f_0 := 1.6 \cdot \text{GHz}$ $f_{\text{bw}} := f_0 \cdot 0.6$ $Z_A := 50 \cdot \Omega$ $p := 1.0$

refer to frequency repetition above. If you need to attenuate signal and all harmonics set to 1.5

Calculate Chebychev (g) Polynomials

$$k := 1..N \quad \mathbf{B} := \ln \left(\coth \left(\frac{L_{\text{ar_db}}}{17.37} \right) \right) \quad ? := \sinh \left(\frac{\mathbf{B}}{2 \cdot N} \right) \quad a_k := \sin \left[\frac{(2 \cdot k - 1) \cdot \mathbf{p}}{2 \cdot N} \right]$$

$$b_k := ?^2 + \left(\sin \left(\frac{k \cdot \mathbf{p}}{N} \right) \right)^2 \quad g_k := 0$$

$$g_0 := 1$$

$$g_{N+1} := 1$$

$g(0)$ and $g(N+1)$ represent the input/output coupling for odd order filters, these are 1 representing the generator (and equal) load resistance

$$g_k := \begin{cases} \frac{2 \cdot a_1}{?} & \text{if } k = 1 \\ \frac{4 \cdot a_{k-1} \cdot a_k}{b_{k-1} \cdot g_{k-1}} & \text{otherwise} \end{cases}$$

$$g = \begin{pmatrix} 1 \\ 1.147 \\ 1.371 \\ 1.975 \\ 1.371 \\ 1.147 \\ 1 \end{pmatrix}$$

Calculate basic factors

$$f_1 := f_0 - \frac{f_{\text{bw}}}{2} \quad a := \cot \left(\frac{\mathbf{p}}{2} \cdot \frac{f_1}{f_0} \right) \quad ? := ? \cdot \mathbf{p} \cdot a$$

$$f_1 = 1.12 \cdot \text{GHz}$$

$$a = 0.509525$$

$$? = 0.509525$$

For N=1. Note the input and output impedances are different

$$N1_{Z_1} := \frac{Z_A}{? \cdot g_0 \cdot g_1} \quad N1_{Z_B} := \frac{Z_A \cdot g_2}{g_0}$$

$$N1_{Z_1} = 85.566 \cdot \text{ohm}$$

$$N1_{Z_B} = 68.56 \cdot \text{ohm}$$

For N=2

$$N2_{Z_1} := Z_A \cdot \left(1 + \frac{1}{? \cdot g_0 \cdot g_1} \right) \quad N2_{Z_{12}} := Z_A \cdot (1 + ? \cdot g_0 \cdot g_1)$$

$$N2_{Z_1} = 135.566 \cdot \text{ohm}$$

$$N2_{Z_{12}} = 79.217 \cdot \text{ohm}$$

$$N2_{Z_2} := \frac{Z_A \cdot g_0}{? \cdot g_2} \quad N2_{Z_B} := Z_A \cdot g_0 \cdot g_3$$

$$N2_{Z_2} = 71.565 \cdot \text{ohm}$$

$$N2_{Z_B} = 98.751 \cdot \text{ohm}$$

For N=3

$$N3_{Z_1} := Z_A \cdot \left(1 + \frac{1}{? \cdot g_0 \cdot g_1} \right) \quad N3_{Z_{12}} := Z_A \cdot (1 + ? \cdot g_0 \cdot g_1)$$

$$N3_{Z_1} = 135.566 \cdot \text{ohm}$$

$$N3_{Z_{12}} = 79.217 \cdot \text{ohm}$$

$$N3_{Z_2} := \frac{Z_A \cdot g_0}{? \cdot g_2} \quad N3_{Z_3} := \frac{Z_A \cdot g_0}{g_4} \cdot \left(1 + \frac{1}{? \cdot g_0 \cdot g_4} \right)$$

$$N3_{Z_2} = 71.565 \cdot \text{ohm}$$

$$N3_{Z_{23}} := \frac{Z_A \cdot g_0}{g_4} \cdot (1 + ? \cdot g_0 \cdot g_1) \quad N3_{Z_B} := \frac{Z_A \cdot g_0}{g_4}$$

$$N3_{Z_{23}} = 57.772 \cdot \text{ohm}$$

$$N3_{Z_3} = 88.655 \cdot \text{ohm}$$

$$N3_{Z_B} = 36.464 \cdot \text{ohm}$$

For N=4

$$N4_{Z_1} := Z_A \cdot \left(2 + \frac{1}{? \cdot g_0 \cdot g_1} \right) \quad N4_{Z_{12}} := Z_A \cdot \left(\frac{1 + 2 \cdot ? \cdot g_0 \cdot g_1}{1 + ? \cdot g_0 \cdot g_1} \right)$$

$$N4_{Z_2} := Z_A \cdot \left[\frac{1}{1 + ? \cdot g_0 \cdot g_1} + \frac{g_0}{? \cdot g_2 (1 + ? \cdot g_0 \cdot g_1)^2} \right] \quad N4_{Z_{23}} := \frac{Z_A}{g_0} \cdot \left(? \cdot g_2 + \frac{g_0}{1 + ? \cdot g_0 \cdot g_1} \right)$$

$$N4_{Z_3} := \frac{Z_A}{? \cdot g_0 \cdot g_3} \quad N4_{Z_{34}} := \frac{Z_A}{g_0 \cdot g_5} \cdot (1 + ? \cdot g_4 \cdot g_5)$$

$$N4_{Z_1} = 185.566 \cdot \text{ohm}$$

$$N4_{Z_4} := \frac{Z_A}{\varepsilon_0 \varepsilon_5} \cdot \left(1 + \frac{1}{? \cdot \varepsilon_4 \cdot \varepsilon_5} \right)$$

$$N4_{Z_B} := \frac{Z_A}{\varepsilon_0 \varepsilon_5}$$

$$N4_{Z_{12}} = 68.441 \cdot \text{ohm}$$

$$N4_{Z_2} = 60.069 \cdot \text{ohm}$$

$$N4_{Z_{23}} = 66.492 \cdot \text{ohm}$$

$$N4_{Z_4} = 98.01 \cdot \text{ohm}$$

$$N4_{Z_3} = 49.686 \cdot \text{ohm}$$

$$N4_{Z_B} = 43.598 \cdot \text{ohm}$$

$$N4_{Z_{34}} = 78.531 \cdot \text{ohm}$$

For N=5

$$N5_{Z_1} := N4_{Z_1} \quad N5_{Z_{12}} := N4_{Z_{12}} \quad N5_{Z_2} := N4_{Z_2} \quad N5_{Z_{23}} := N4_{Z_{23}} \quad N5_{Z_3} := N4_{Z_3}$$

$$N5_{Z_4} := \frac{Z_A}{\varepsilon_0} \cdot \left[\frac{1}{1 + ? \cdot \varepsilon_5 \cdot \varepsilon_6} + \frac{\varepsilon_6}{? \cdot \varepsilon_4 (1 + ? \cdot \varepsilon_4 \cdot \varepsilon_5)^2} \right]$$

$$N5_{Z_{34}} := \frac{Z_A}{\varepsilon_0} \cdot \left(? \cdot \varepsilon_4 + \frac{\varepsilon_6}{1 + ? \cdot \varepsilon_5 \cdot \varepsilon_6} \right)$$

$$N5_{Z_5} := \frac{Z_A \cdot \varepsilon_6}{\varepsilon_0} \cdot \left(2 + \frac{1}{? \cdot \varepsilon_5 \cdot \varepsilon_6} \right)$$

$$N5_{Z_{45}} := \frac{Z_A \cdot \varepsilon_6}{\varepsilon_0} \cdot \left(\frac{1 + 2 \cdot ? \cdot \varepsilon_5 \cdot \varepsilon_6}{1 + ? \cdot \varepsilon_5 \cdot \varepsilon_6} \right)$$

$$N5_{Z_1} = 185.566 \cdot \text{ohm}$$

$$N5_{Z_{12}} = 68.441 \cdot \text{ohm}$$

$$N5_{Z_B} := \frac{Z_A \cdot \varepsilon_6}{\varepsilon_0}$$

$$N5_{Z_4} = 53.616 \cdot \text{ohm}$$

$$N5_{Z_2} = 60.069 \cdot \text{ohm}$$

$$N5_{Z_{45}} = 68.441 \cdot \text{ohm}$$

$$N5_{Z_{23}} = 66.492 \cdot \text{ohm}$$


$$N5_{Z_5} = 185.566 \cdot \text{ohm}$$

$$N5_{Z_3} = 49.686 \cdot \text{ohm}$$

$$N5_{Z_B} = 50 \cdot \text{ohm}$$

$$N5_{Z_{34}} = 66.492 \cdot \text{ohm}$$

Does it work?

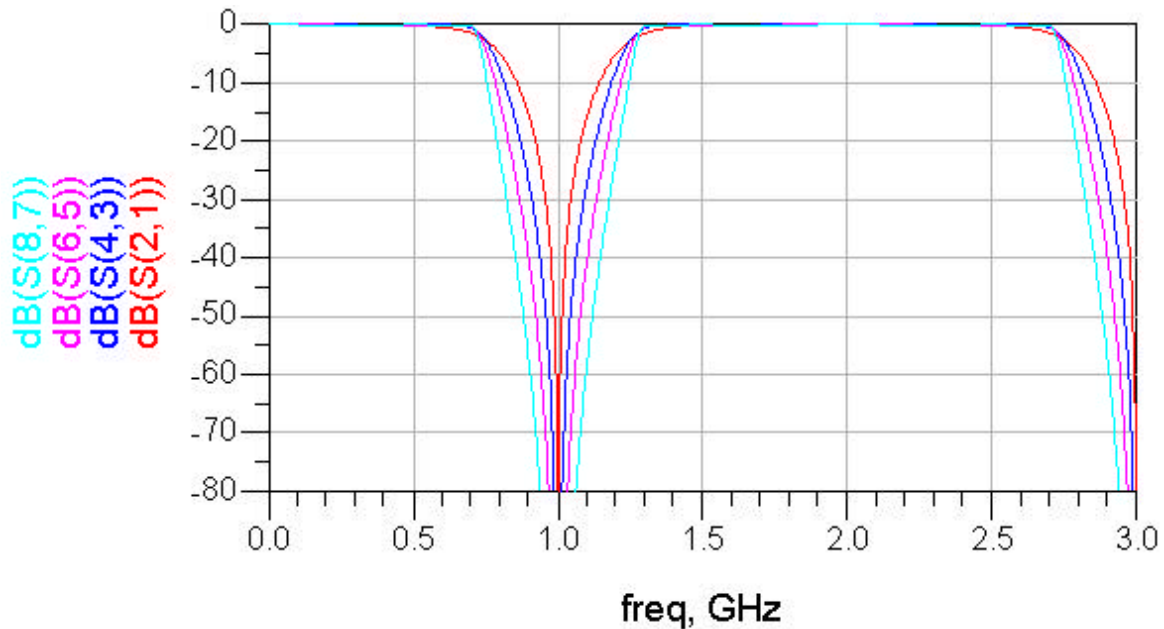

The plots above are for four different notch filters from $n=2$ to $n=5$, simulated with ideal transmission lines shown below. Each line is 90 degrees at the wanted frequency, and the results are in excellent agreement.

